


Lets say the strain gauge causes a compression (and tension) of 10% strain. This means the length was decreased (or increased, in case of tension) by 10%.

Resistivity of Copper = $1.724 \times 10^{-8} \Omega m$

$$\text{Poisson's Ratio of Copper} = 0.36 = \frac{\delta \epsilon_{trans}}{\delta \epsilon_{axial}} = \frac{\delta \epsilon_{trans}}{0.1}$$

$$\delta \epsilon_{trans} = 0.36 \times 0.1 = 0.036$$

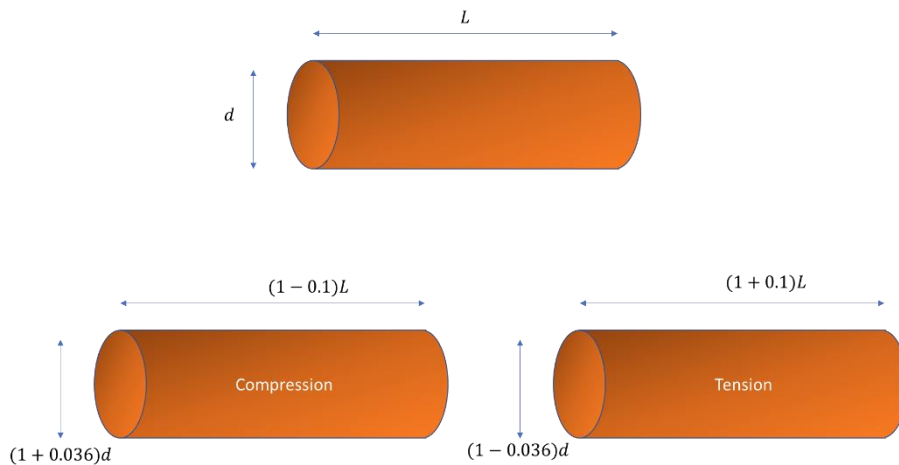This means, if the length of the conductor increased by 10% (or 0.1), the diameter decreased by 3.6% (or 0.036). Similarly, for compression.



Now how does that translate to change in resistance?

$$R = \rho \frac{L}{A} = \rho \frac{L}{\pi r^2} = \rho \frac{4L}{\pi D^2} = \frac{4\rho}{\pi} \frac{L}{D^2}$$

Lets solve for compression,


$$R_{comp} = \frac{4\rho}{\pi} \frac{0.9L}{(1.036D)^2} = \frac{4\rho}{\pi} \frac{0.9L}{1.0733D^2} = 0.838 \frac{4\rho}{\pi} \frac{L}{D^2} = 0.838R$$

Similarly, for tension,

$$R_{tens} = \frac{4\rho}{\pi} \frac{1.1L}{(0.964D)^2} = \frac{4\rho}{\pi} \frac{1.1L}{0.9292D^2} = 1.183 \frac{4\rho}{\pi} \frac{L}{D^2} = 1.183R$$

This means, the resistance dropped to 83.8% of original value (or, by 16.2%) under compression, and increased to 118.3% of original value (or, by 18.3%).

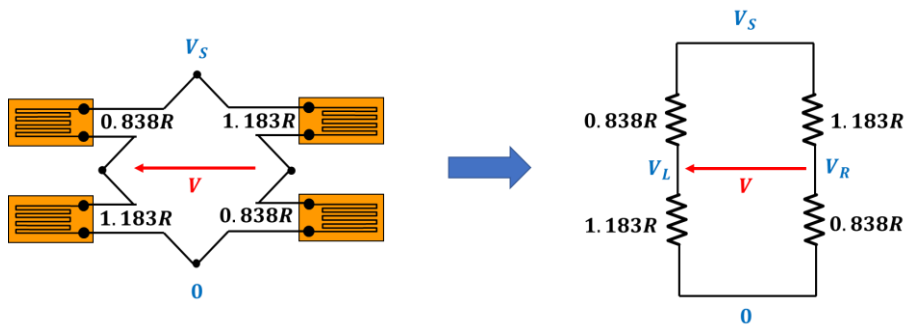The Wheatstone Bridge would look something as follows:




Using the familiar equation for a potentiometer,

$$V_L = V_S \frac{1.183R}{0.838R + 1.183R} = \frac{1.183R}{2.021R} = 0.585V_S$$

$$V_R = V_S \frac{0.838R}{0.838R + 1.183R} = \frac{0.838R}{2.021R} = 0.415V_S$$

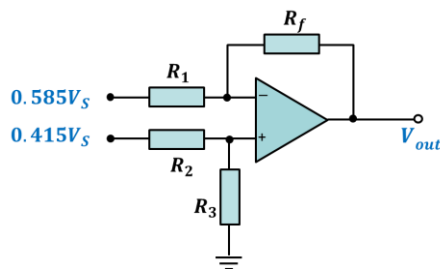So, a voltage is produced which can be amplified with the Op-Amp.



Now, we must solve the op amp circuit. Here are the equations we can start with:

1. $V_{out} = A(V_+ - V_-)$
2. $V_+ = \frac{R_3}{R_2 + R_3} 0.415 V_S$
3. $\frac{0.585 V_S - V_-}{R_1} = \frac{V_- - V_{out}}{R_f}$

Solving equation (3) further to isolate V_- :

$$\begin{aligned} \frac{0.585 V_S - V_-}{R_1} &= \frac{V_- - V_{out}}{R_f} \\ \Rightarrow 0.585 R_f V_S - R_f V_- &= R_1 V_- - R_1 V_{out} \\ \Rightarrow 0.585 R_f V_S + R_1 V_{out} &= R_1 V_- + R_f V_- \\ \Rightarrow \frac{0.585 R_f V_S + R_1 V_{out}}{R_1 + R_f} &= V_- \end{aligned}$$

Now, we can replace the Op-Amp input voltage values in the open-loop gain equation (1):

$$V_{out} = A(V_+ - V_-)$$

$$\begin{aligned} \Rightarrow V_{out} &= A \left(\frac{R_3}{R_2 + R_3} 0.415 V_s - \frac{0.585 R_f V_s + R_1 V_{out}}{R_1 + R_f} \right) \\ \Rightarrow V_{out} + A \frac{R_1 V_{out}}{R_1 + R_f} &= A \left(\frac{0.415 R_3}{R_2 + R_3} V_s - \frac{0.585 R_f V_s}{R_1 + R_f} \right) \\ \Rightarrow V_{out} \left(1 + A \frac{R_1}{R_1 + R_f} \right) &= V_s \left(A \frac{0.415 R_3}{R_2 + R_3} - A \frac{0.585 R_f}{R_1 + R_f} \right) \end{aligned}$$

Dividing both sides by A:

$$\Rightarrow V_{out} \left(\frac{1}{A} + \frac{R_1}{R_1 + R_f} \right) = V_s \left(\frac{0.415 R_3}{R_2 + R_3} - \frac{0.585 R_f}{R_1 + R_f} \right)$$

Since $A \gg 1$, we can easily replace $\frac{1}{A} \approx 0$:

$$\Rightarrow V_{out} \left(\frac{R_1}{R_1 + R_f} \right) = V_s \left(\frac{0.415 R_3}{R_2 + R_3} - \frac{0.585 R_f}{R_1 + R_f} \right)$$

Above is the worked mathematics to solve a problem like this. As you see, it is simply Kirchhoff's Laws and simple maths! Let's produce a general equation using $\delta\epsilon_{axial}$ (instead of 10%).

$$R_{comp} = \frac{4\rho}{\pi} \frac{(1 - \delta\epsilon_{axial})L}{(1 + \nu\delta\epsilon_{axial})^2 D^2} = \frac{(1 - \delta\epsilon_{axial})}{(1 + \nu\delta\epsilon_{axial})^2} R$$

$$R_{tens} = \frac{4\rho}{\pi} \frac{(1 + \delta\epsilon_{axial})L}{(1 - \nu\delta\epsilon_{axial})^2 D^2} = \frac{(1 + \delta\epsilon_{axial})}{(1 - \nu\delta\epsilon_{axial})^2} R$$

Then, we find the voltage produced across the Wheatstone Bridge as a result:

$$\begin{aligned} V_L &= V_s \frac{\frac{(1 + \delta\epsilon_{axial})}{(1 - \nu\delta\epsilon_{axial})^2} R}{\frac{(1 - \delta\epsilon_{axial})}{(1 + \nu\delta\epsilon_{axial})^2} R + \frac{(1 + \delta\epsilon_{axial})}{(1 - \nu\delta\epsilon_{axial})^2} R} \\ \Rightarrow V_L &= V_s \frac{\frac{(1 + \delta\epsilon_{axial})(1 + \nu\delta\epsilon_{axial})^2}{(1 - \nu\delta\epsilon_{axial})^2(1 + \nu\delta\epsilon_{axial})^2}}{\frac{(1 - \delta\epsilon_{axial})(1 - \nu\delta\epsilon_{axial})^2 + (1 + \delta\epsilon_{axial})(1 + \nu\delta\epsilon_{axial})^2}{(1 + \nu\delta\epsilon_{axial})^2(1 - \nu\delta\epsilon_{axial})^2}} \\ \Rightarrow V_L &= V_s \frac{(1 + \delta\epsilon_{axial})(1 + \nu\delta\epsilon_{axial})^2}{(1 - \delta\epsilon_{axial})(1 - \nu\delta\epsilon_{axial})^2 + (1 + \delta\epsilon_{axial})(1 + \nu\delta\epsilon_{axial})^2} \end{aligned}$$

Similarly,

$$V_R = V_s \frac{(1 - \delta\epsilon_{axial})(1 - \nu\delta\epsilon_{axial})^2}{(1 - \delta\epsilon_{axial})(1 - \nu\delta\epsilon_{axial})^2 + (1 + \delta\epsilon_{axial})(1 + \nu\delta\epsilon_{axial})^2}$$